

CORRIENTE ALTERNA y RESONANCIA

L, R y C

RLC serie \rightarrow oscilador amortiguado

$$\left(\frac{R}{2L}\right)^2 \quad \frac{1}{LC}$$

$$L \rightarrow \text{nuclear} \quad , \quad V_L = L \frac{dI}{dt}$$

$$C \rightarrow \text{nuclearística} \quad \frac{1}{C} \quad , \quad V_C = \frac{Q}{C}$$

$$R \rightarrow \text{dissipación} \quad V_R = I \cdot R$$

- $V = V_0 \cos(\omega t)$

$$R) \quad I_R = \frac{V_0}{R} \cos(\omega t)$$

$$L) \quad V_L = L \frac{dI}{dt} \quad \rightarrow \quad \int \frac{V}{L} dt = \int dI$$

$$\frac{V_0}{L\omega} \sin(\omega t) = I$$


$$\frac{V_0}{L\omega} \cos(\omega t - \frac{\pi}{2}) = I$$

$$C) \quad V_C = \frac{Q}{C} \quad \rightarrow \quad \frac{dV}{dt} = \frac{dQ}{dt} \cdot \frac{1}{C} = \frac{I}{C}$$

$$I = C \frac{dV}{dt} = C \frac{d}{dt} (V_0 \cos(\omega t)) \\ = -C \omega V_0 \sin(\omega t)$$

$$I_C = \underbrace{C \omega V_0}_{I_0(\omega)} \cos(\omega t + \frac{\pi}{2})$$
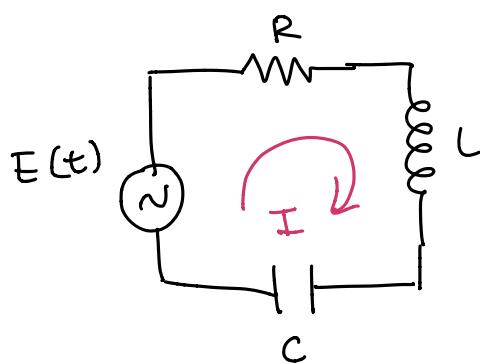
$$V = \text{cte} \rightarrow V \text{ con } \omega \ll 1$$



$$E(t) = E_0 \cdot \cos(\omega t)$$

$$IR + L \frac{dI}{dt} + \frac{1}{C} I = E(t)$$


sol. homogénea $\rightarrow 0$

$$\tau \approx \frac{2L}{R}$$

sol. particular

$$I(t) = I_0 \cos(\omega t + \phi)$$
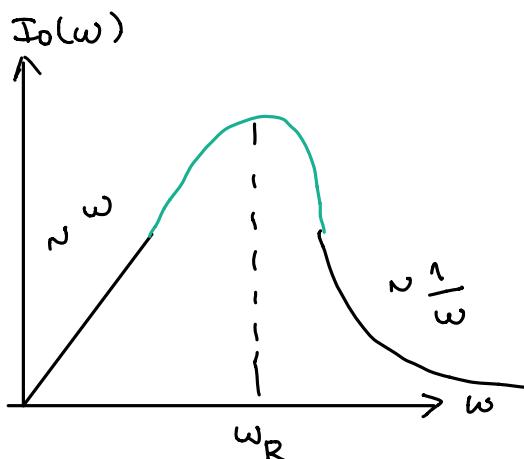
$$\begin{cases} I_0 = I_0(\omega) \\ \phi = \phi(\omega) \end{cases} \leftarrow$$



$$I_0 = \frac{E_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$\tan \phi = \frac{\omega L - 1/\omega C}{R}$$

$$I_{max} = I_0(\omega_R) \Rightarrow \omega L - \frac{1}{\omega C} = 0$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC} \equiv \omega_0^2$$

$$\hookrightarrow I_{max} = \frac{E_0}{R}$$

$$\tan \phi(\omega_R) = 0 \rightarrow \phi = 0$$

ancho a mitad de altura de la potencia

$$P_{max} \propto I^2 \quad \text{busco } \omega \text{ tq } P = \frac{P_{max}}{2} \propto \frac{I^2}{2}$$

$$\Rightarrow I_0(\omega) = \frac{I_{max}}{\sqrt{2}}$$

$$I_0 = \frac{E_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} = \frac{E_0}{R \sqrt{1 + \frac{1}{R^2} (\omega L - \frac{1}{\omega C})^2}}$$

$$\Rightarrow \frac{I_0}{I_{max}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow 1 + \frac{1}{R^2} (\omega L - \frac{1}{\omega C})^2 = 2$$


$$R^2 = (\omega L - \frac{1}{\omega C})^2$$

$$\Leftrightarrow |\omega L - \frac{1}{\omega C}| = R$$

$\omega > 0$

- $\omega_+ = \frac{R}{ZL} + \sqrt{\left(\frac{R}{ZL}\right)^2 + \omega_0^2}$

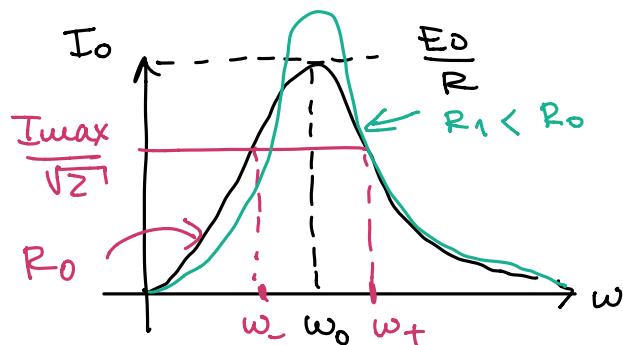- $\omega_- = -\frac{R}{ZL} + \sqrt{\left(\frac{R}{ZL}\right)^2 + \omega_0^2}$



auch

$$\begin{aligned} \Delta\omega &= \omega_+ - \omega_- \\ &= \frac{R}{ZL} - \left(-\frac{R}{ZL}\right) \\ \Delta\omega &= \frac{R}{L} \end{aligned}$$

radio AM 1000 kHz

$$\text{RLC} \rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\frac{1}{\sqrt{LC}} = \omega_0 \rightarrow f_0 = \frac{1}{2\pi} \omega_0 = \frac{1}{2\pi\sqrt{LC}} = 1000 \text{ kHz} \leftarrow$$

$$\Delta\omega = 100 \text{ kHz}$$

$\nearrow -$

$$1050 \text{ kHz} \leftarrow$$